

Chip 18
like
(#53)

$$\Delta V = \sum \mathcal{E} - I r$$

$$120 = \mathcal{E} - 15r \quad 120 = \mathcal{E} - 15(4)$$


$$-100 = -\mathcal{E} + 20r \quad 120 = \mathcal{E} - 60$$

$$20 = 5r \quad \mathcal{E} = 180$$

$$r = 4 \Omega$$

like chap 18 ④ $R_T = 2\Omega + 2\frac{2}{3}\Omega = 10\frac{2}{3}\Omega$

#45

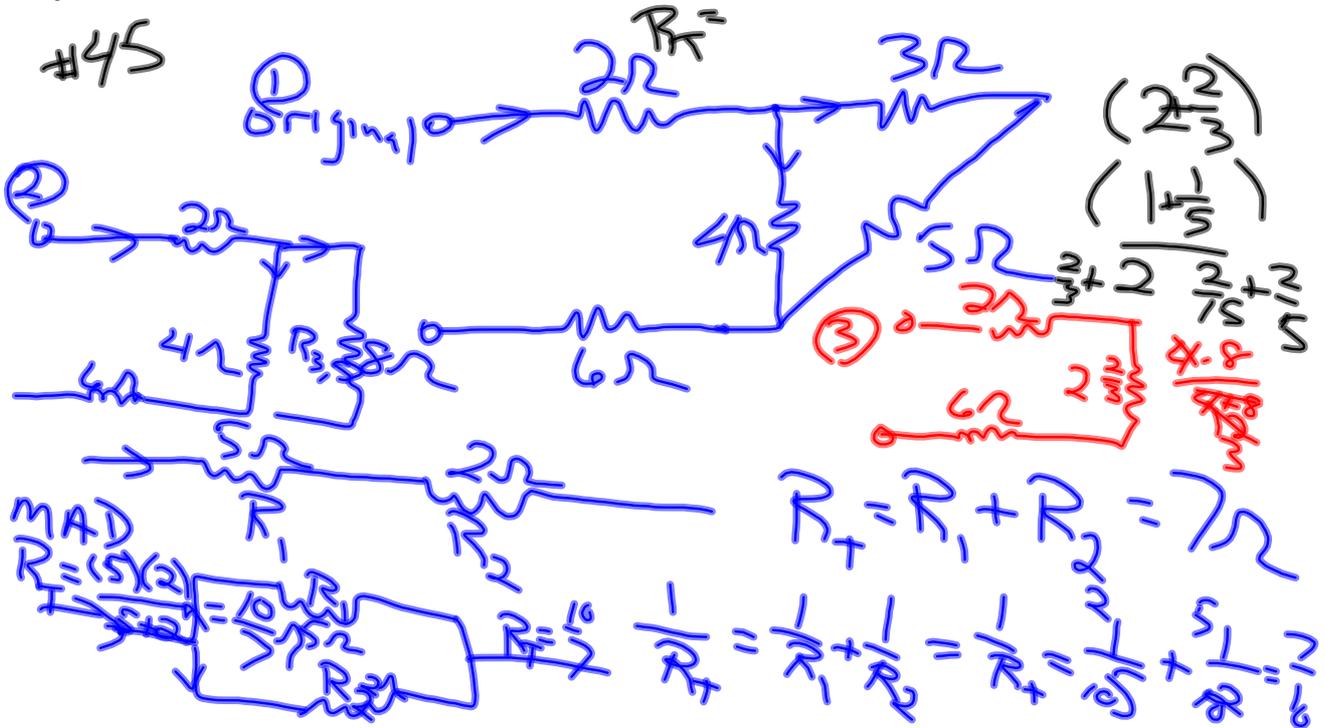

$$A = \begin{bmatrix} 1 & -1 & -1 \\ 6 & 0 & 24 \\ 0 & -12 & 24 \end{bmatrix}_{3 \times 3} \quad B = \begin{bmatrix} 0 \\ 42 \\ 0 \end{bmatrix}_{3 \times 1}$$

$$I_6 - I_{12} - I_{24} = 0$$

$$6I_6 + 0I_{12} + 24I_{24} = 42$$

$$0I_6 - 12I_{12} + 24I_{24} = 0$$

$$\cancel{A} X = \cancel{A} B \quad X = \underbrace{A^{-1}}_{3 \times 3} \underbrace{B}_{3 \times 1} = \underbrace{\quad}_{3 \times 1}$$



#16

42
 -18
 \hline
 24

$\Delta V = IR = (3A)(8\Omega) = 24V$
 $\Delta V = IR = (1A)(24\Omega) = 24V$

$-12I_{12} + 24I_{24} - 24I_{24} = 0$
 $24V = I_{12} \cdot 12\Omega$
 $I_{12} = \frac{24V}{12\Omega} = 2A$
 $24V = I_{24} \cdot 24\Omega$
 $I_{24} = \frac{24V}{24\Omega} = 1A$

$I_6 = ?$
 $I_{12} = ?$
 $I_{24} = ?$

$42 + 6I_6 + 24I_{24} = 0$

$R_T = R + 6\Omega = 12 + 24 = 36\Omega$
 $R_T = 36\Omega + 6\Omega = 42\Omega$

$I_T = \frac{V_T}{R_T} = \frac{42V}{14\Omega} = 3A$



$I_6 = I_{12} + I_{24}$

$I_6 + I_{12} = I_{24}$

$I_6 + I_{12} + I_{24} = ?$

Chp 18
11

$R_+ = 75 \Omega$
 $R = ?$

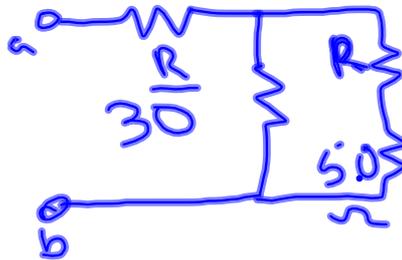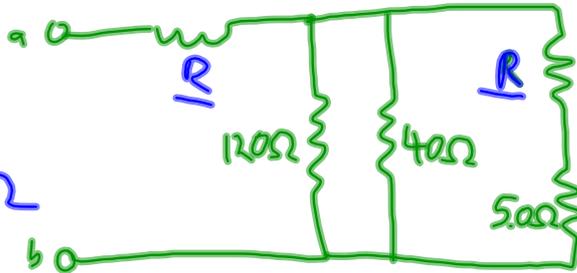

$$R_p = \frac{120 \times 40}{120 + 40} = \frac{160}{4}$$

